



The input voltage for the AC small signal actually only needs to be 1 volt at the positive terminal and 0 volts at the negative terminal, as the assistant mentioned. Using this square root of 2 thing is just for switching the voltage entirely, and it's basically unrelated to what the task requires. Providing a voltage exceeding the square root of 2 won't actually render the small signal model inapplicable. However, when using the square root of 2 AC input signal voltage, it is also acceptable as long as you adhere to the principle of having "one side positive and one side negative."

Vov=2.559-1.65=0.909
abs (small sig.) = sqrt(0.4) * 0.5749020786
unit = V

806.0mv on branch Vo is Steady-state voltage.
Steady-state voltage => Vac=0.
The following two statements are incorrect;
I found out after asking the teaching assistant.:
DC gain : (?)
 $20 \log (709.1 \times 10^{-3} / 0.5749020786) = 1.82227213$

Title		
ELE3HW1-1		
Size	Document Number	Rev
A	E24074724	1.0.0
Date:	Friday, September 15, 2023	Sheet 1 of 1